



DT – Year 5 Autumn 2  
**Electrical Systems-Flood  
 Warning System**  
 (Previous knowledge –basic electrical  
 systems)

Vocabulary

Tier 1	Tier 2	Tier 3
water	circuit	Series circuit
switch	sensor	conductivity
flood	current	Parallel circuit
battery	voltage	resistor
alarm	connection	Monitoring system

don't know  
 I know this word  
 I can use it in a sentence

Health and Safety

- Remove any jewellery and tie back long hair. Wear an apron.
- Do not put fingers or objects in outlets.
- Never use anything with a plug, wire or cord around water.
- Keep metal objects away from electrical heat sources – e.g. knife away from toaster.
- Never pull a plug out by its cord.
- Follow electrical signs and guidance carefully.
- Return all equipment to the correct zoned areas of the classroom/ workshop.
- Remember that electricity can cause burns, shocks, serious injury & even death.


**Project: Flood Warning Systems**

This half term you will learn:


- the key components used to create a functioning circuit;
- the difference between series and parallel circuits;
- why breaks in a circuit will stop it from working;
- to make a working circuit, select, and use the appropriate materials;
- to create a flood warning system referring to the design criteria;
- to map out where different components will go in the system
- design a flood warning system with a simple electrical circuit;
- to create a labelled design showing positive and negative parts in relation to the LED and the battery.



**Technical Knowledge**

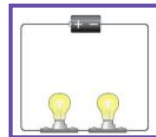

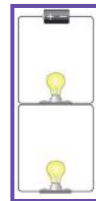This is a diagram of a **series circuit** – the electrical current flows through every component in the circuit – the switch, battery and bulbs.



This is a diagram of a **parallel circuit** – this has two or more paths for the electrical current to flow through. If one loop is disconnected then the other still has power.

*Which type of circuit will you use in your flood warning system?*

**Key Knowledge**

Electricity travels at the speed of light, that's 300 million metres per second! However, the electricity that flows through your home and appliances you use is much slower, about 1/100th the speed of light.



A traditional light bulb has a filament that heats up and glows when an electrical current runs through it. Up to 90% of the energy used goes towards producing the heat.



Useful Resources

Circuit construction kit:  
[https://phet.colorado.edu/sims/html/circuit-construction-kit-dc/latest/circuit-construction-kit-dc\\_en.html](https://phet.colorado.edu/sims/html/circuit-construction-kit-dc/latest/circuit-construction-kit-dc_en.html)

<p>Research</p>	<p>Design</p>	<p>Make</p>	<p>Evaluate</p>
-----------------	---------------	-------------	-----------------